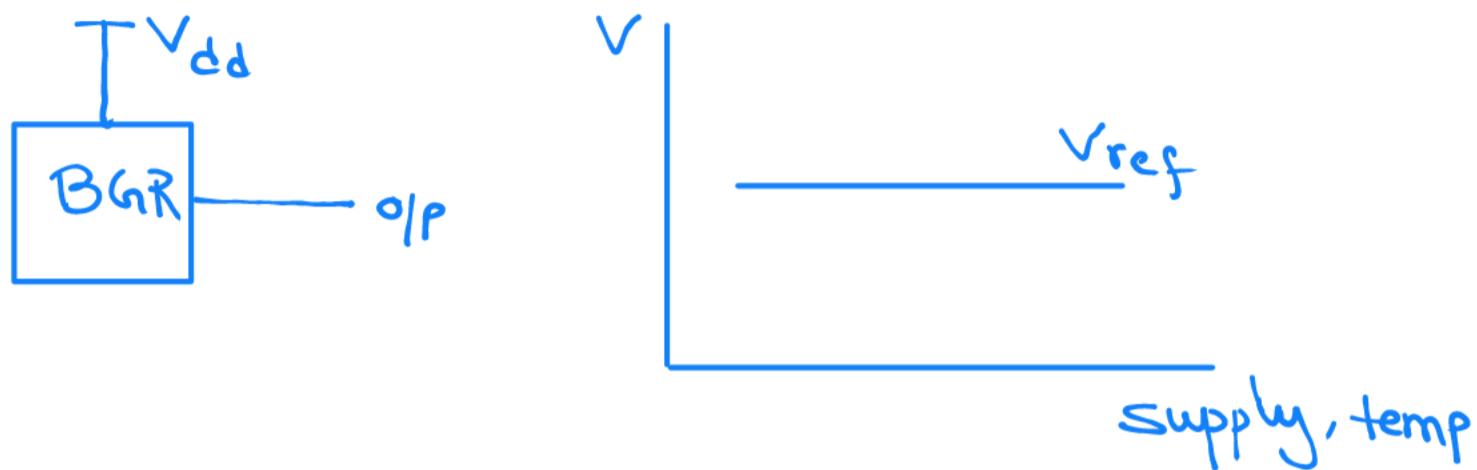




Bandgap Reference Circuit

Bandgap Reference


→ Constant Reference voltage Independent of supply & Temperature variation.




Used: LDO, Buck
ADC, DAC

Industry std. Temp. variation : -40° to 125°C
Supply variation: 10%, 20%....

1. Supply Variation
2. Temp. Variation

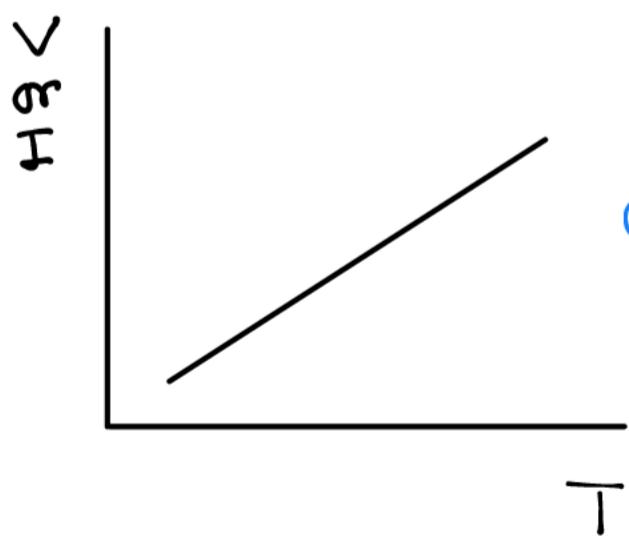


PTAT
(Prop. to Absolute Temp)

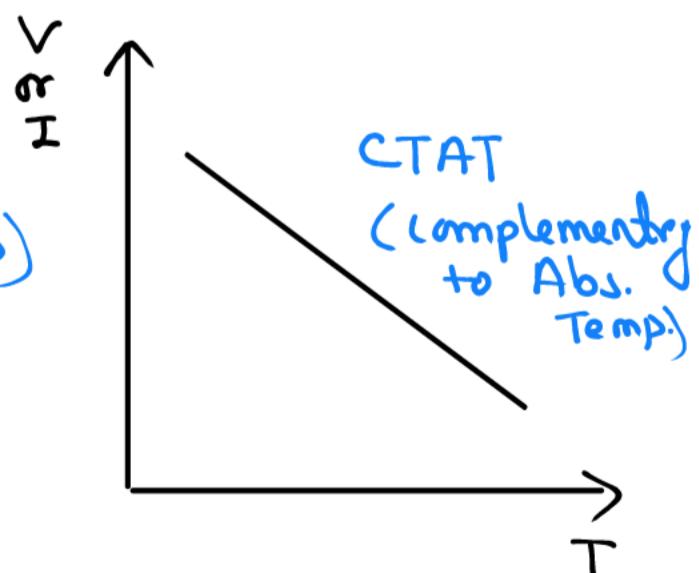


CTAT
(Complementary to Abs. Temp.)

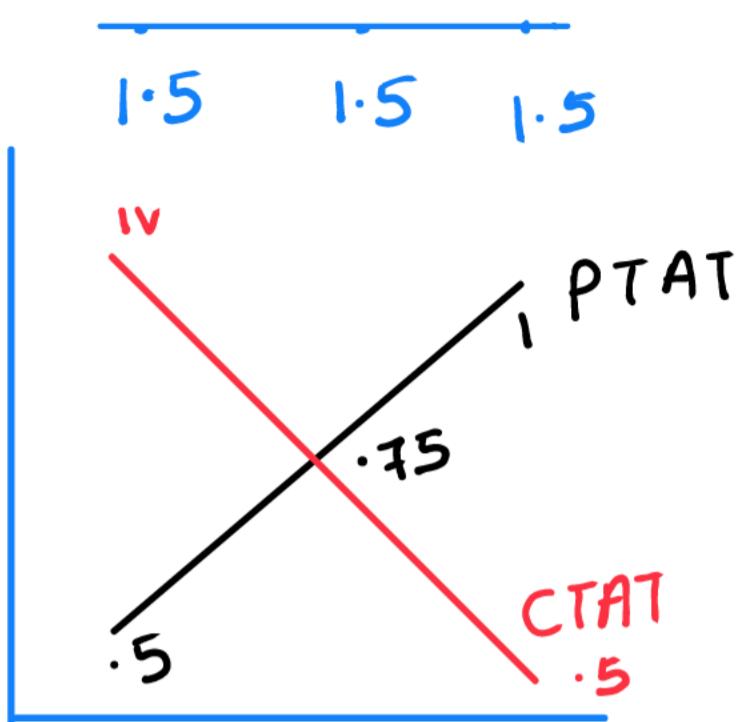$\text{PTAT} + \text{CTAT} = \text{Constant Voltage}$




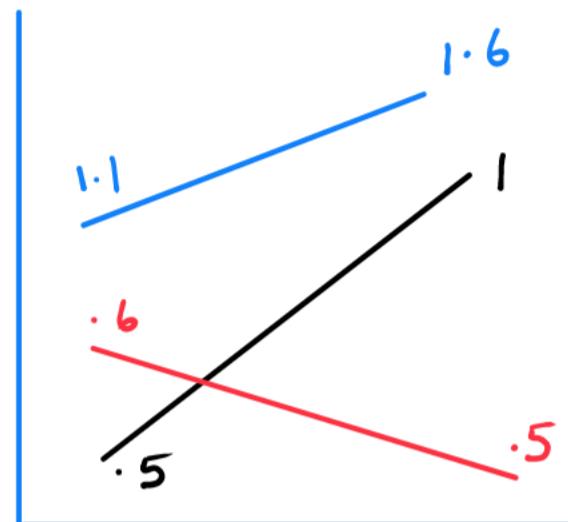$\text{Any PTA} + \text{Any CTAT} \neq \text{const. Voltage}$





But, $\alpha_1 \text{PTAT} + \alpha_2 \text{CTAT}$
= Const. Voltage.

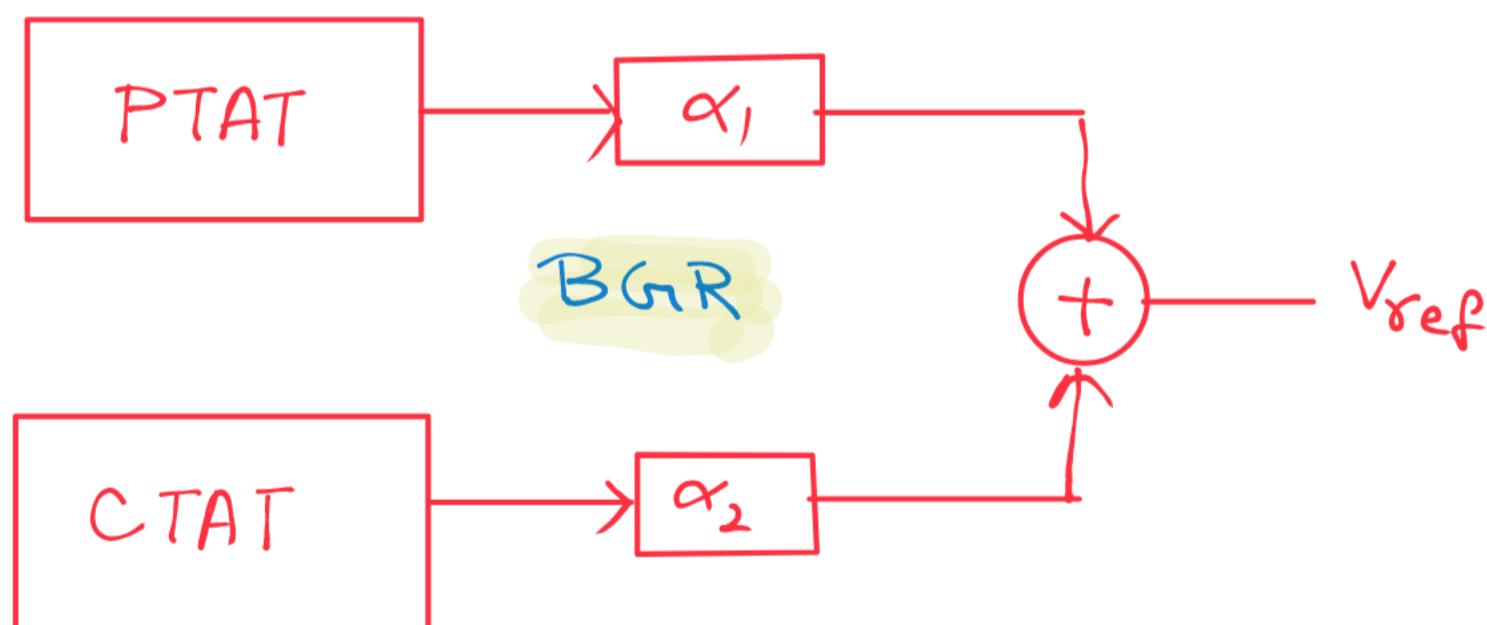→ Adjusting α_1 & α_2 , we can get constant voltages.



Design of BGR

CTAT

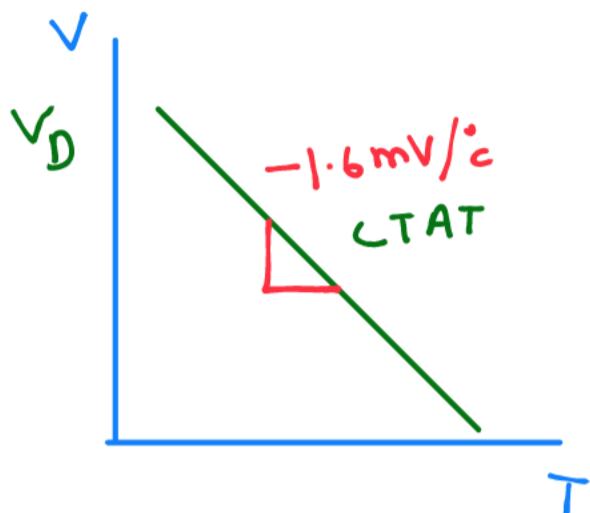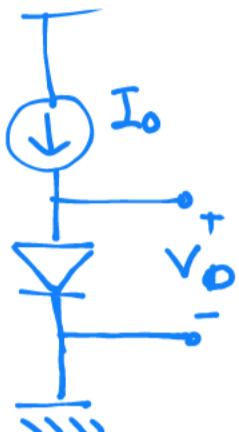

$$I_0 = \text{const.} / \text{temp, supply}$$

$$I_0 = I_s e^{V_D/V_t}$$

V_t = Thermal voltage

$$= 26 \text{ mV}/300\text{K}$$

I_s = reverse bias sat. current

$$V_D = V_t \ln \left(\frac{I_0}{I_s} \right)$$

(1)

voltage across the diode decreases with temp. at a rate of $-1.6 \text{ mV/}^\circ\text{C}$. (when const. current is passing)

$$V_D = V_t \ln \left(\frac{I_0}{I_s} \right)$$

$$\frac{\partial V_D}{\partial T} = -1.6 \text{ mV/}^\circ\text{C}$$

$$V_t = \frac{kT}{q} \propto T \quad (\text{PTAT})$$

$\ln \left(\frac{I_0}{I_s} \right)$ (CTAT) "dominate"

Now, $I_0 \rightarrow \text{constant}$

$$\frac{\partial I_0}{\partial T} = 0$$

$$\frac{\partial V_D}{\partial T} = \frac{k}{q} \quad (2)$$

$$I_s \propto \mu K T n_i^2$$

$$n_i^2 \propto T^m ; m = -3/2$$

$$n_i^2 \propto T^3 \exp \left[-\frac{E_g}{kT} \right]$$

$$I_s \propto b T^m \cdot T \cdot T^3 \exp \left[-\frac{E_g}{kT} \right]$$

$$I_s = b T^{(4+m)} \exp \left[-\frac{E_g}{kT} \right] \quad (3)$$

$$I_s = b T^{(4+m)} \exp\left[-\frac{E_g}{kT}\right]$$

$$\frac{\partial I_s}{\partial T} = b \left[T^{(4+m)} \left(e^{-E_g/kT} \right) - \frac{E_g}{k} \cdot \frac{1}{T^2} + (4+m) T^{3+m} \left(e^{-E_g/kT} \right) \right]$$

$$= b \left(e^{-E_g/kT} \right) \left[T^{4+m} \frac{E_g}{kT^2} + (4+m) T^{3+m} \right]$$

$$= b e^{-E_g/kT} T^{4+m} \left[\frac{E_g}{kT^2} + \frac{4+m}{T} \right]$$

$$\frac{\partial I_s}{\partial T} = I_s \left[\frac{E_g}{kT^2} + \frac{4+m}{T} \right] \quad \text{--- (4)}$$

$$V_D = V_T \ln\left(\frac{I_0}{I_s}\right) \quad \text{--- (1)}$$

$$\frac{\partial V_D}{\partial T} = f(V_T, I_s) \quad \frac{\partial V_T}{\partial T} \text{ & } \frac{\partial I_s}{\partial T}$$

$$\frac{\partial V_D}{\partial T} = \frac{\partial V_T}{\partial T} \ln\left(\frac{I_0}{I_s}\right) + V_T \frac{\partial}{\partial T} \ln\left(\frac{I_0}{I_s}\right)$$

$$= \frac{\partial V_T}{\partial T} \ln\left(\frac{I_0}{I_s}\right) + \frac{V_T}{I_0/I_s} - \frac{I_0}{I_s^2} \frac{\partial I_s}{\partial T}$$

$$= \underbrace{\frac{\partial V_T}{\partial T} \ln\left(\frac{I_0}{I_s}\right)}_{(2)} - V_T \frac{1}{I_s} \frac{\partial I_s}{\partial T} \underbrace{\frac{1}{I_0}}_{(4)}$$

$$= \frac{k}{q} \ln\left(\frac{I_0}{I_s}\right) - V_T \frac{1}{I_s} \cancel{I_s} \left[\frac{E_g}{kT^2} + \frac{4+m}{T} \right]$$

$$= \frac{V_T}{T} \ln\left(\frac{I_0}{I_s}\right) - \frac{V_T}{T} (4+m) - \frac{V_T E_g}{kT^2}$$

$$\frac{\partial V_D}{\partial T} = \frac{V_D}{T} - \frac{V_T(4+m)}{T} - \frac{kT}{q} \frac{E_g}{kT^2}$$


$$= \frac{V_D}{T} - \frac{V_T(4+m)}{T} - \frac{E_g}{2T}$$

$$\boxed{\frac{\partial V_D}{\partial T} = \frac{V_D - V_T(4+m) - E_g/2}{T}}$$


$$\frac{\partial V_D}{\partial T} = \frac{0.7 - (4-3/2)26mV - 1.2}{300^\circ K}$$

$$= \frac{0.7 - 5mV - 1.2}{300^\circ K} = -1.6mV/K$$



$$=-1.88 \text{ mV/K}$$

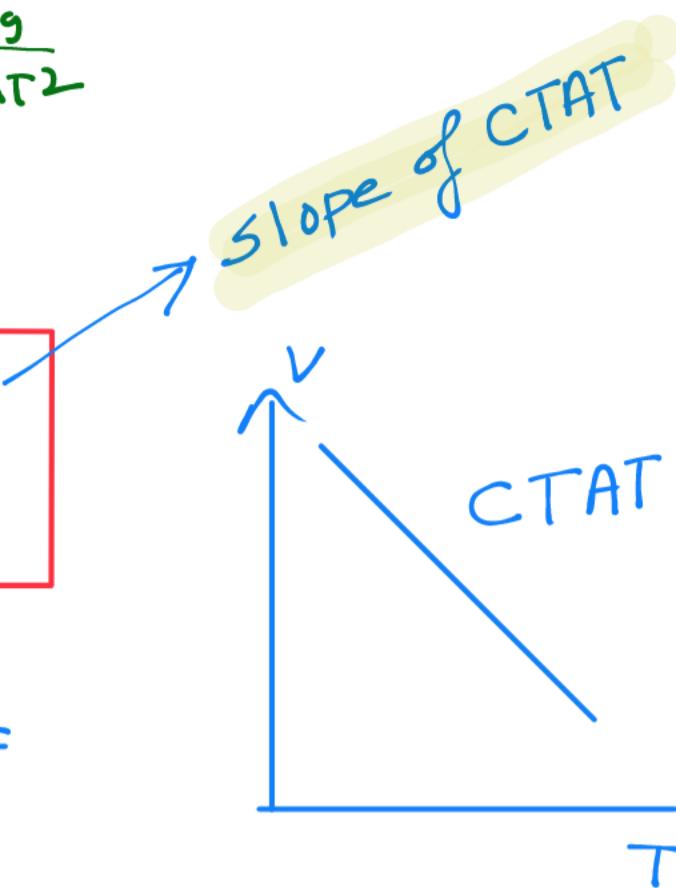

How to make diode in CMOS Process

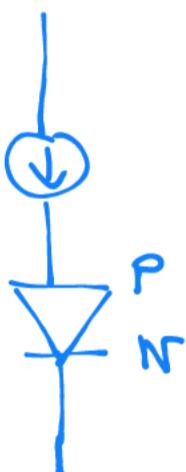


"This implementation is not sufficient"

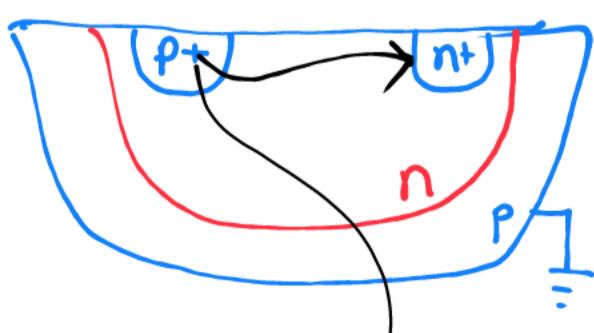
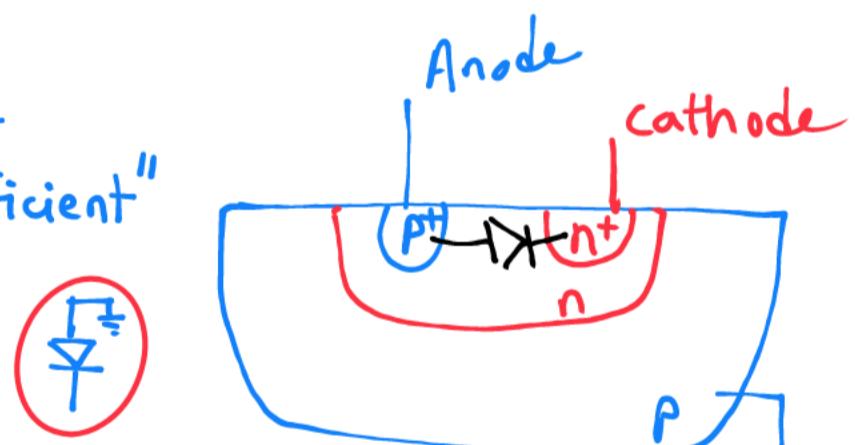


X leakage through sub.

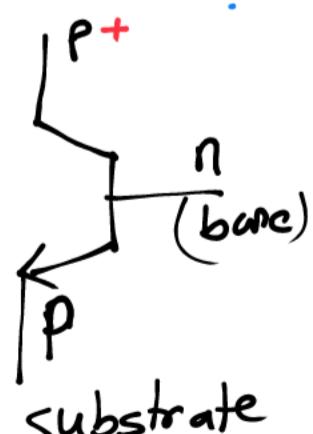base current
leads to large collector current



Parasitic BJT.

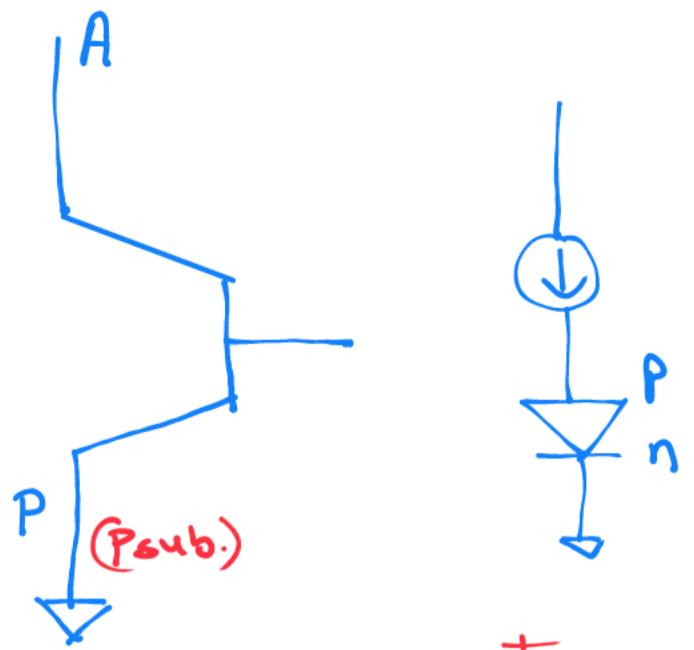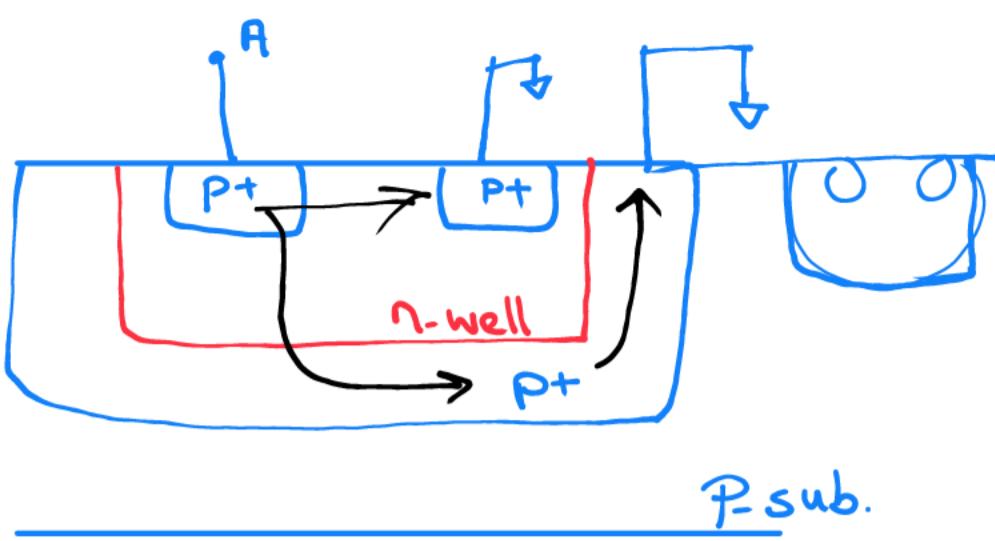

"No substrate current"


Whenever we want to make diode ckt in CMOS technology, due to various disadvantages, we ended up with parasitic BJT. (can't avoid to form pnp)

The current which was flowing through the substrate, in this p+ region was created to collect the current, place


so, other mosfets are not affected by substrate current

DC Sweep

Sweep variable : Temp. (-40 to 125)

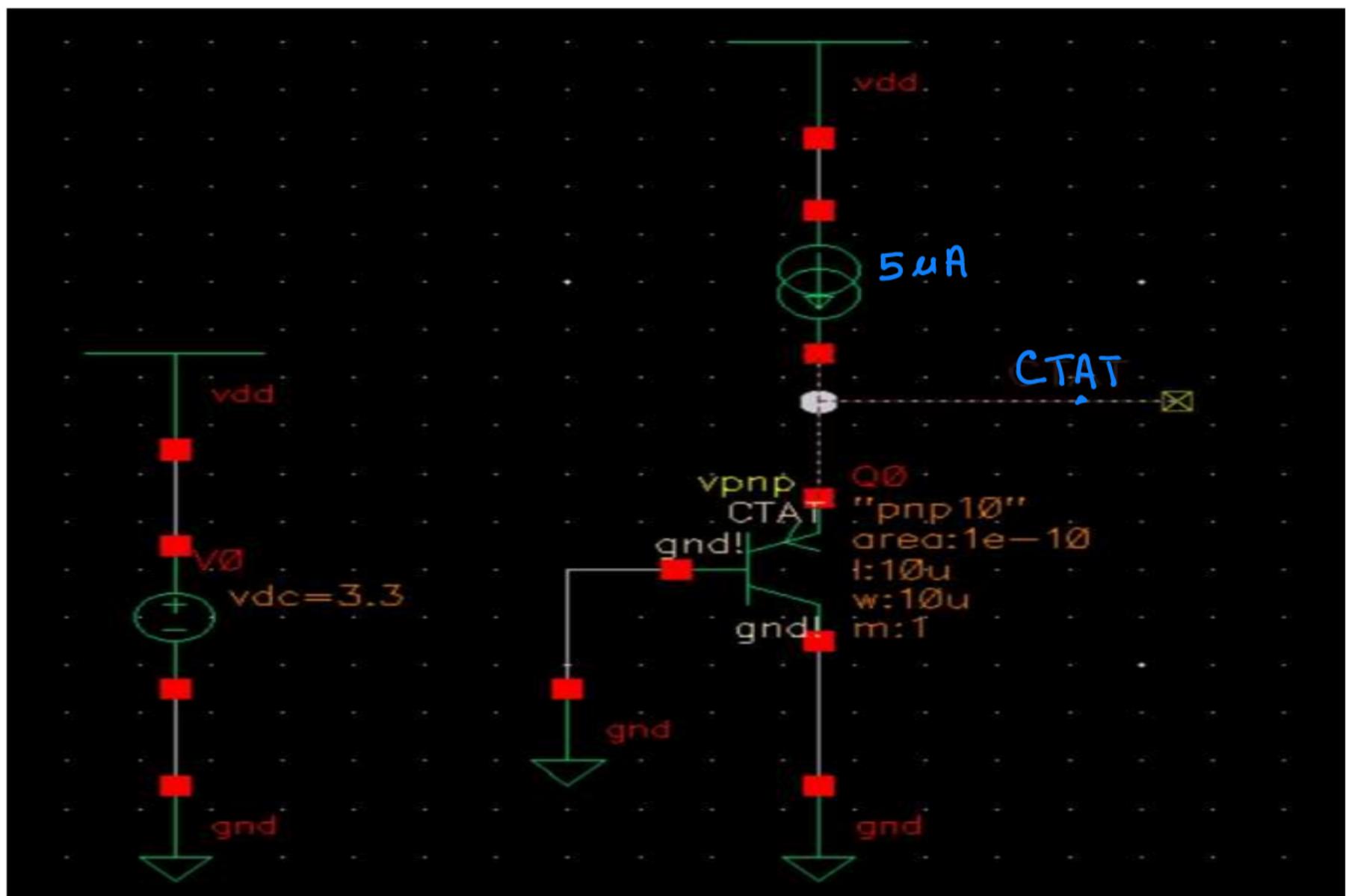

output @ CTAT:

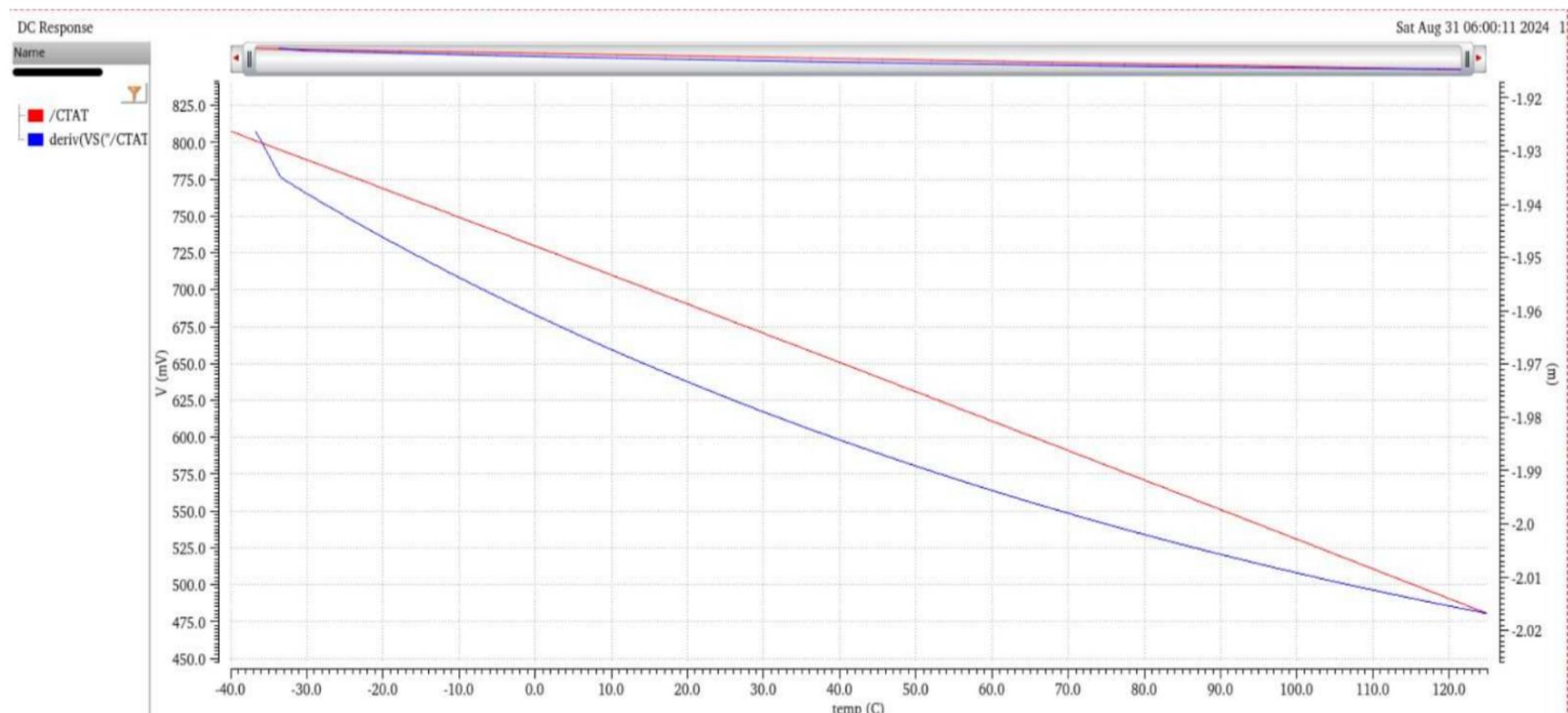

PTAT


$$V_T = \frac{kT}{q}$$

$$V_T \propto T$$


$$V_D = V_T \ln \left(\frac{I_0}{I_S} \right)$$

PTAT CTAT

eliminate $I_S = ?$

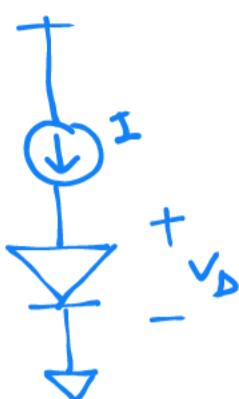

Array of Diodes (n)

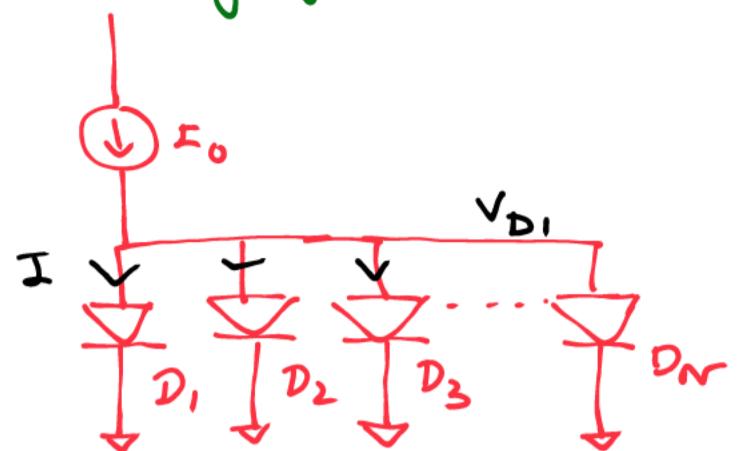

$$V_D - V_{D1} = ?$$

$$I = I_S e^{V_D/V_T}$$

$$I_0 = nI$$

$$\Rightarrow I_0 = n I_S e^{V_{D1}/V_T}$$

$$\Rightarrow V_{D1} = V_T \ln \left(\frac{I_0}{n I_S} \right)$$

$$\& V_D = V_T \ln \left(\frac{I_0}{I_S} \right)$$

$$\therefore V_D - V_{D1}$$

$$= V_T \left(\ln \frac{I_0}{I_S} - \ln \frac{I_0}{n I_S} \right)$$

$$= V_T \ln \left(\frac{I_0}{I_S} \times \frac{n I_S}{I_0} \right)$$

$$= V_T \ln(n)$$

$$V_D - V_{D1} = V_T \ln(n)$$

constant.

→ PTAT (As $V_T = \frac{kT}{q}$)


Circuit Implementation of these expressions:

Assumption: $V_D = V_2$ Same current I_0

$$V_D = I_0 R + V_{D1}$$

$$\Rightarrow I_0 R = V_D - V_{D1} = V_T \ln(n)$$

PTAT

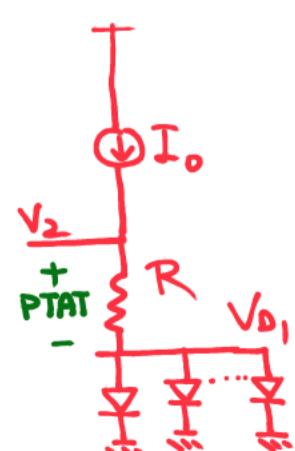

- ① Current Mirror
② Op-amp.

} Two ways:


$$I_{Dm_1} = I_{Dm_2}$$

$$\Rightarrow k_n' \left(\frac{W}{L}\right) \left(\frac{V_{gs_1} - V_t}{2}\right)^2 = k_n' \left(\frac{W}{L}\right) \left(V_{gs_2} - V_t\right)^2$$

$$\Rightarrow V_{gs_1} = V_{gs_2}$$

$$\Rightarrow V_{s_1} = V_{s_2} \text{ (source is same)}$$



$$\therefore V_D = V_2$$

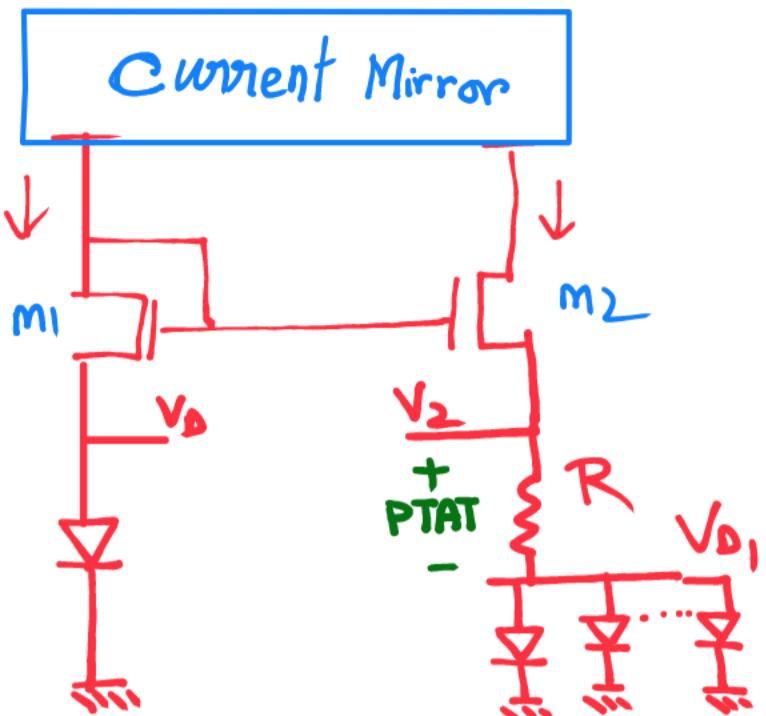

$$I_o R_i = V_T \ln(N)$$

PTAT

Const

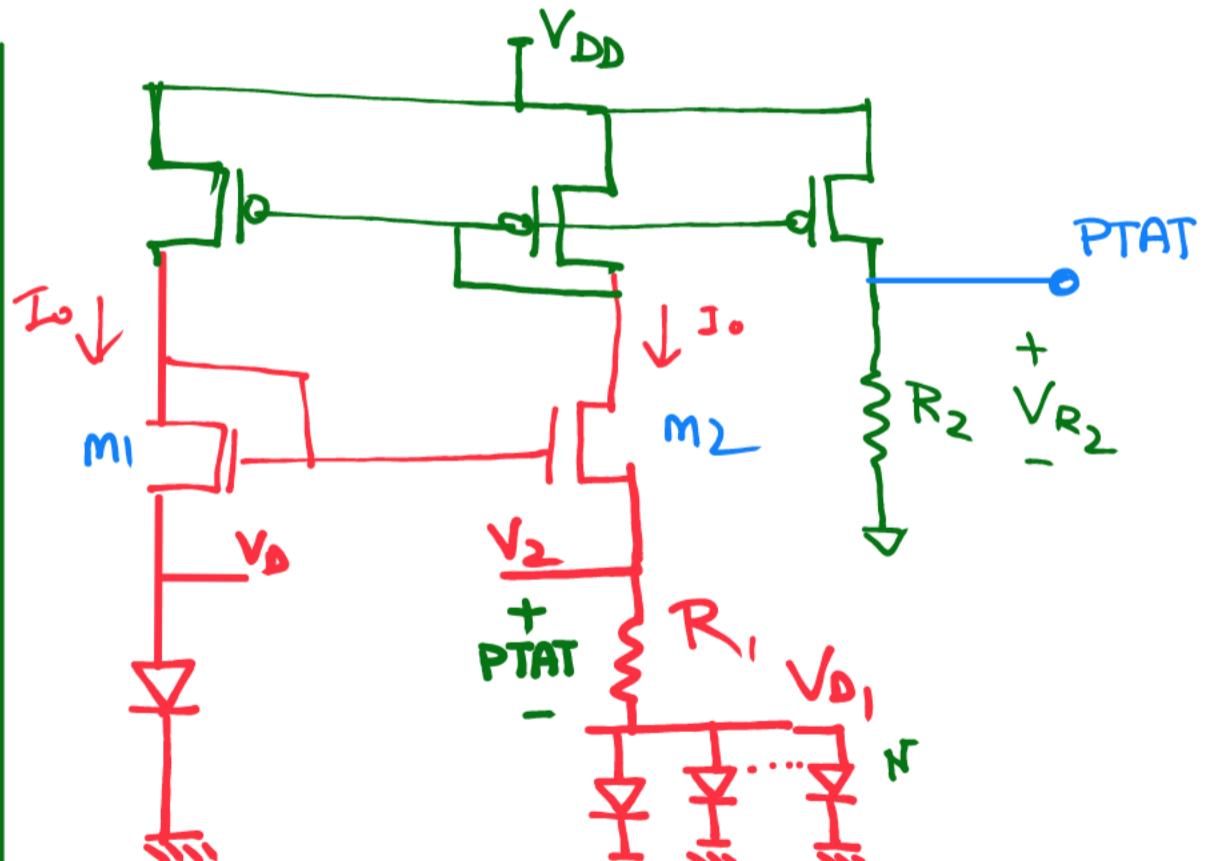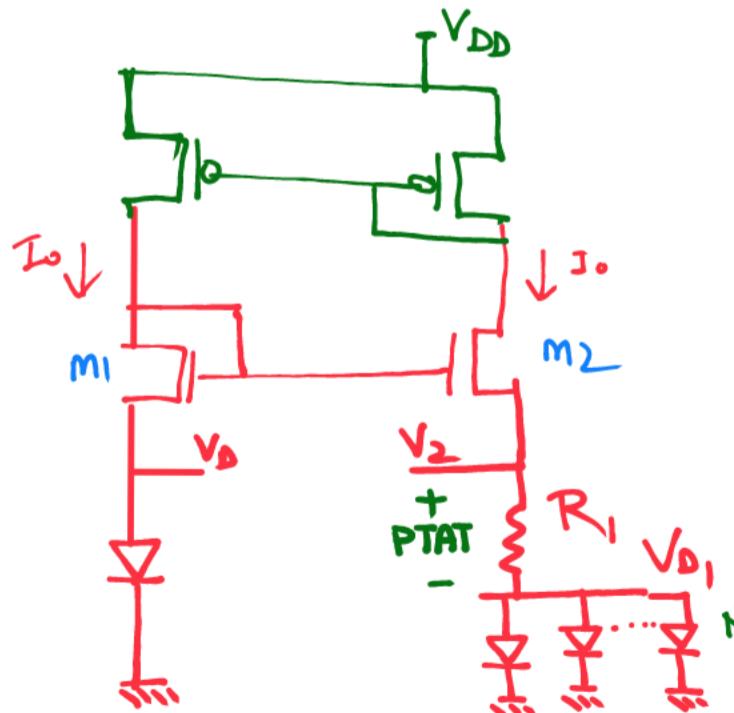

$$I_o R_i = V_T \ln(N)$$

$$I_o = \frac{V_T}{R_i} \ln(N)$$

$$V_{R2} = \frac{R_2}{R_1} V_T \ln(N)$$

ratio

const

PTAT

$$V_{R_2} = \frac{R_2}{R_1} \ln(N) V_T$$


α_1 PTAT

$$\frac{\partial V_{R_2}}{\partial T} = \frac{R_2}{R_1} \ln(N) \frac{\partial V_T}{\partial T}$$

$$\frac{\partial V_T}{\partial T} = \frac{k}{q^2} = \frac{1.38 \times 10^{-23}}{1.6 \times 10^{-19}}$$

$$= 86.25 \mu\text{V}/^\circ\text{K}$$

$$87 \quad 85$$

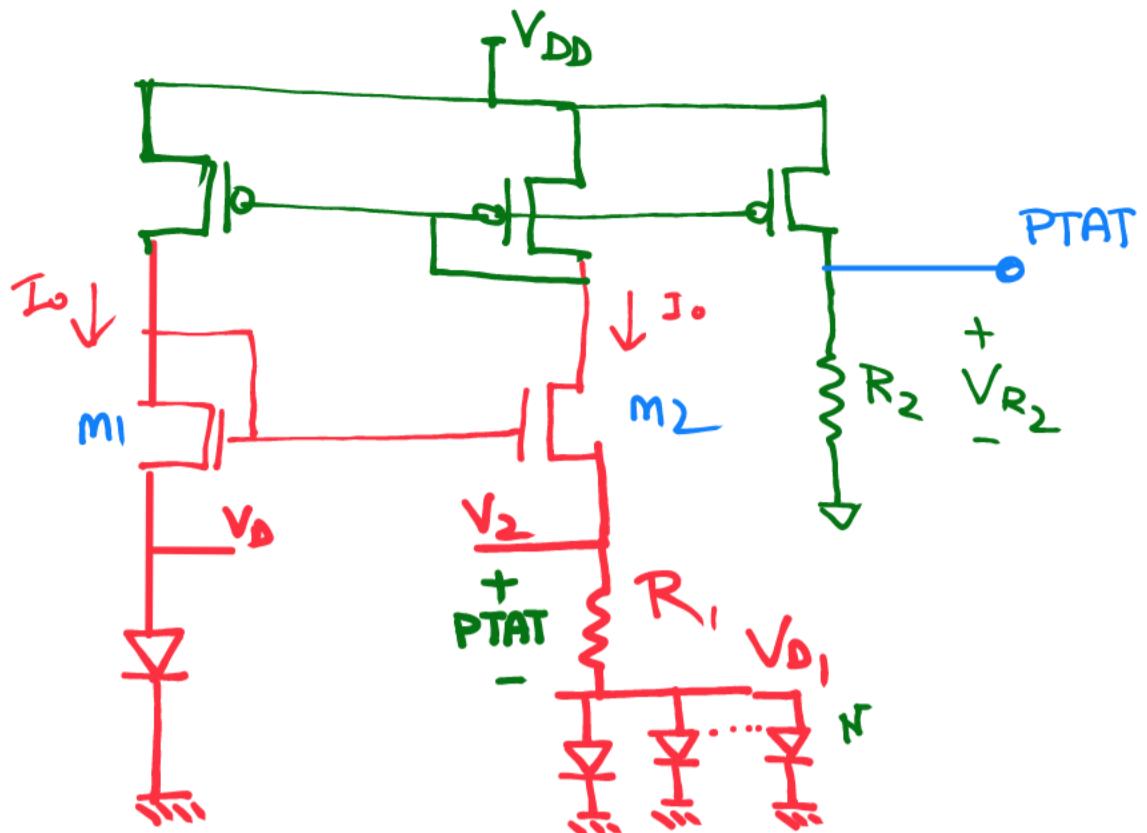

$$\frac{\partial}{\partial T}(\text{CTAT}) = -1.6 \text{ mV}/^\circ\text{K}$$

$$\frac{\partial}{\partial T}(\text{PTAT}) = 85 \mu\text{V}/^\circ\text{K}$$

Used large W & L \rightarrow to reduce the effect of process variation.


$$R_L = \frac{V_T \ln(N)}{I}$$

$N=2$
 $I = 5\mu A$


$$= \frac{0.026 \times \ln(2)}{5\mu}$$

$$= 3.6 k\Omega$$


Schematic :

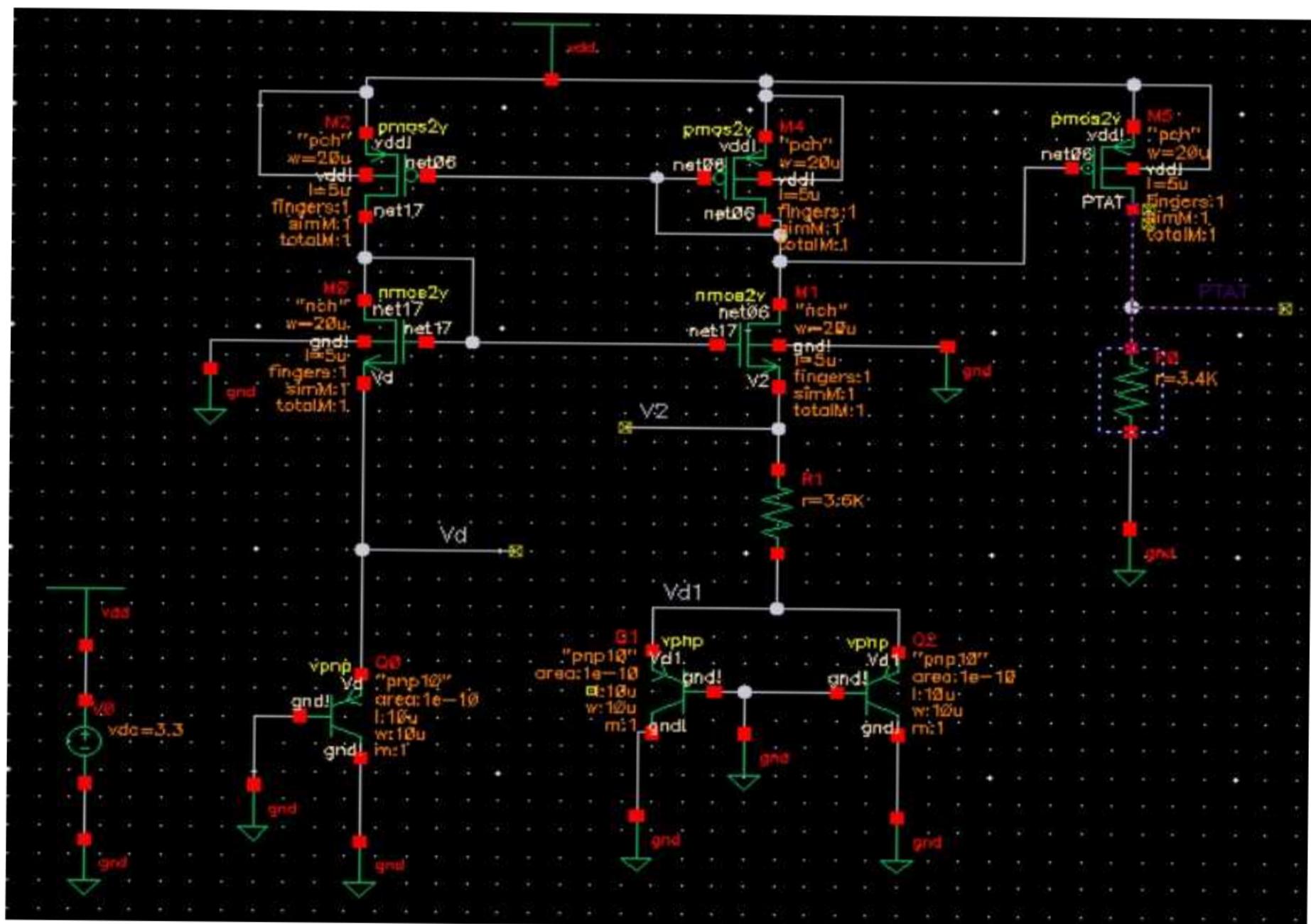


$V_d - V_{d\downarrow} :$

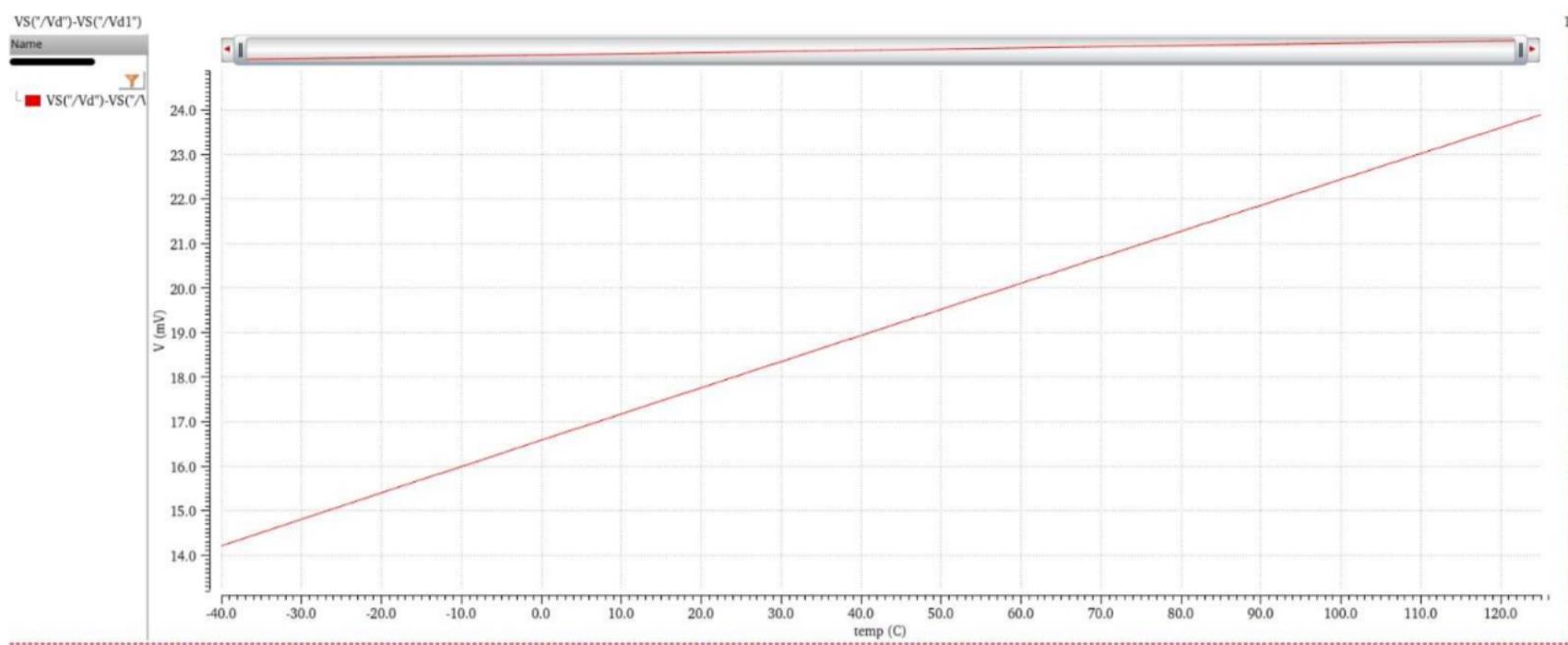

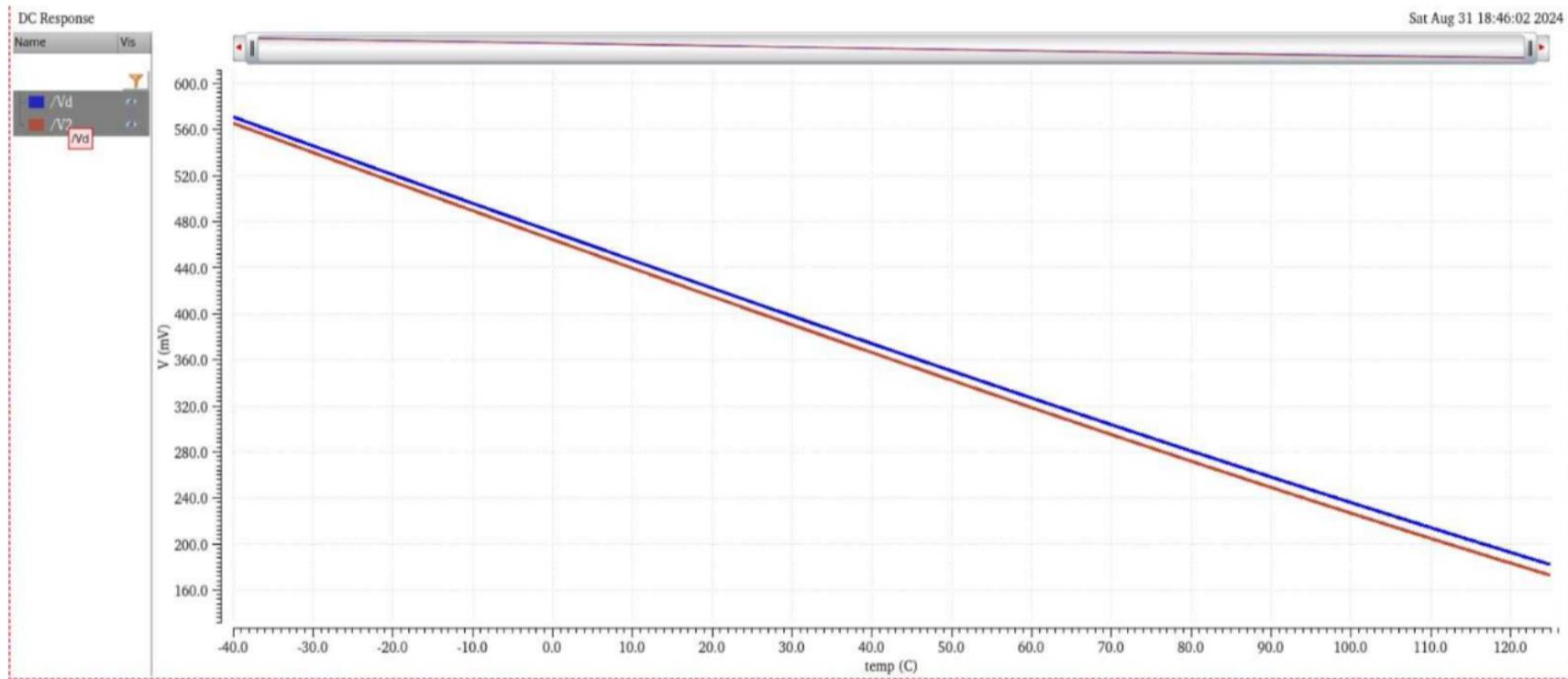
$V_2 \approx V_d$ (nearly $R_1 = 3.6 \text{ k}\Omega$) :




Current across M_0 & M_1 mosfets:

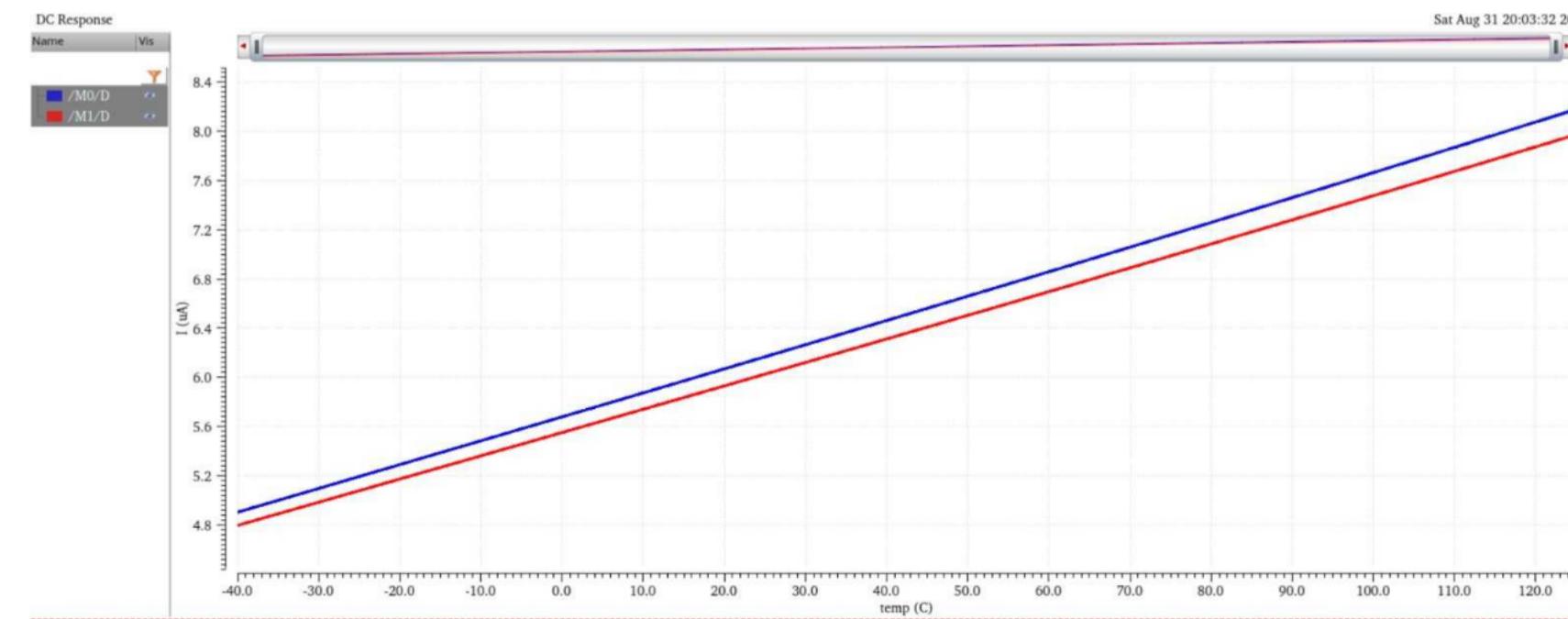


$V_2 - V_{d1}$:

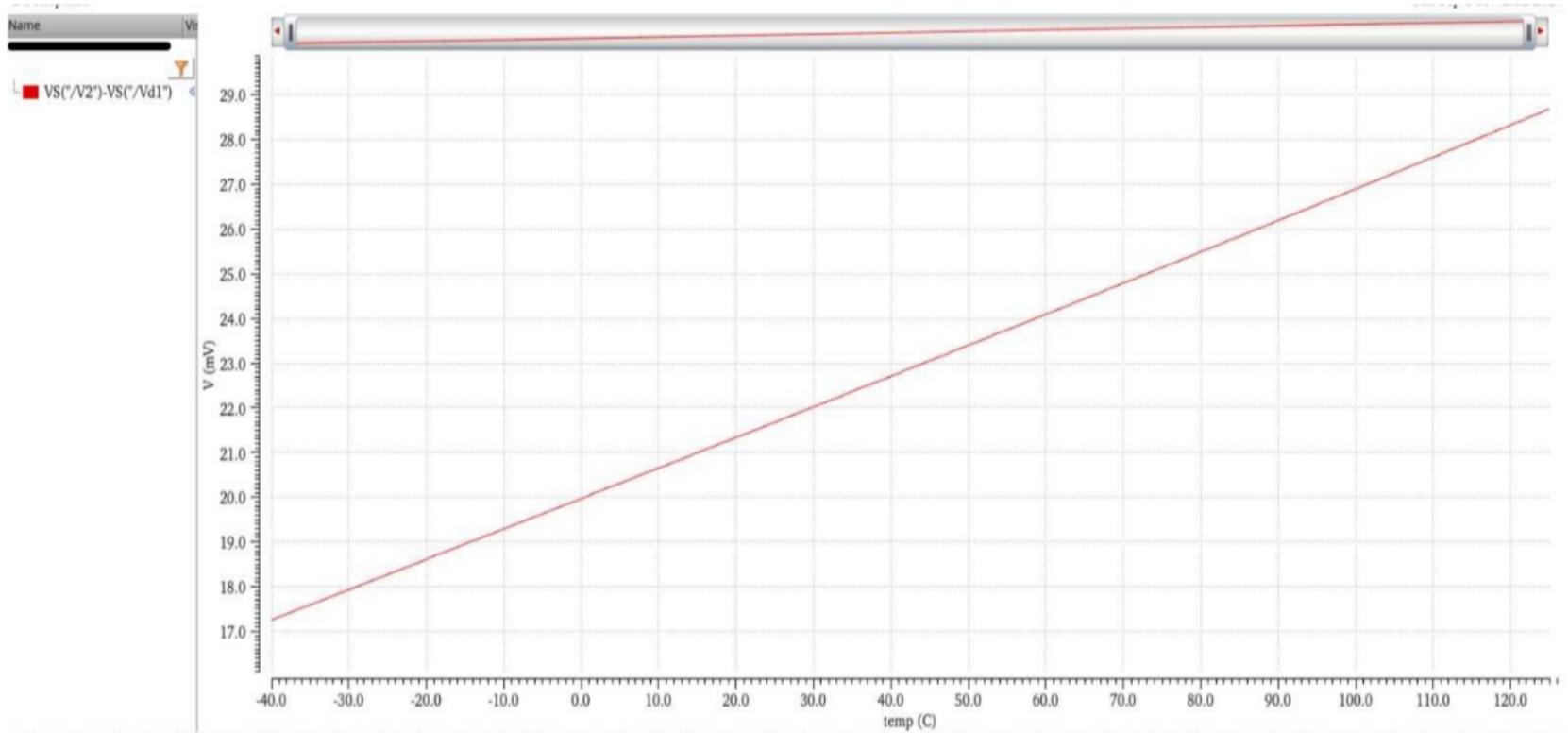

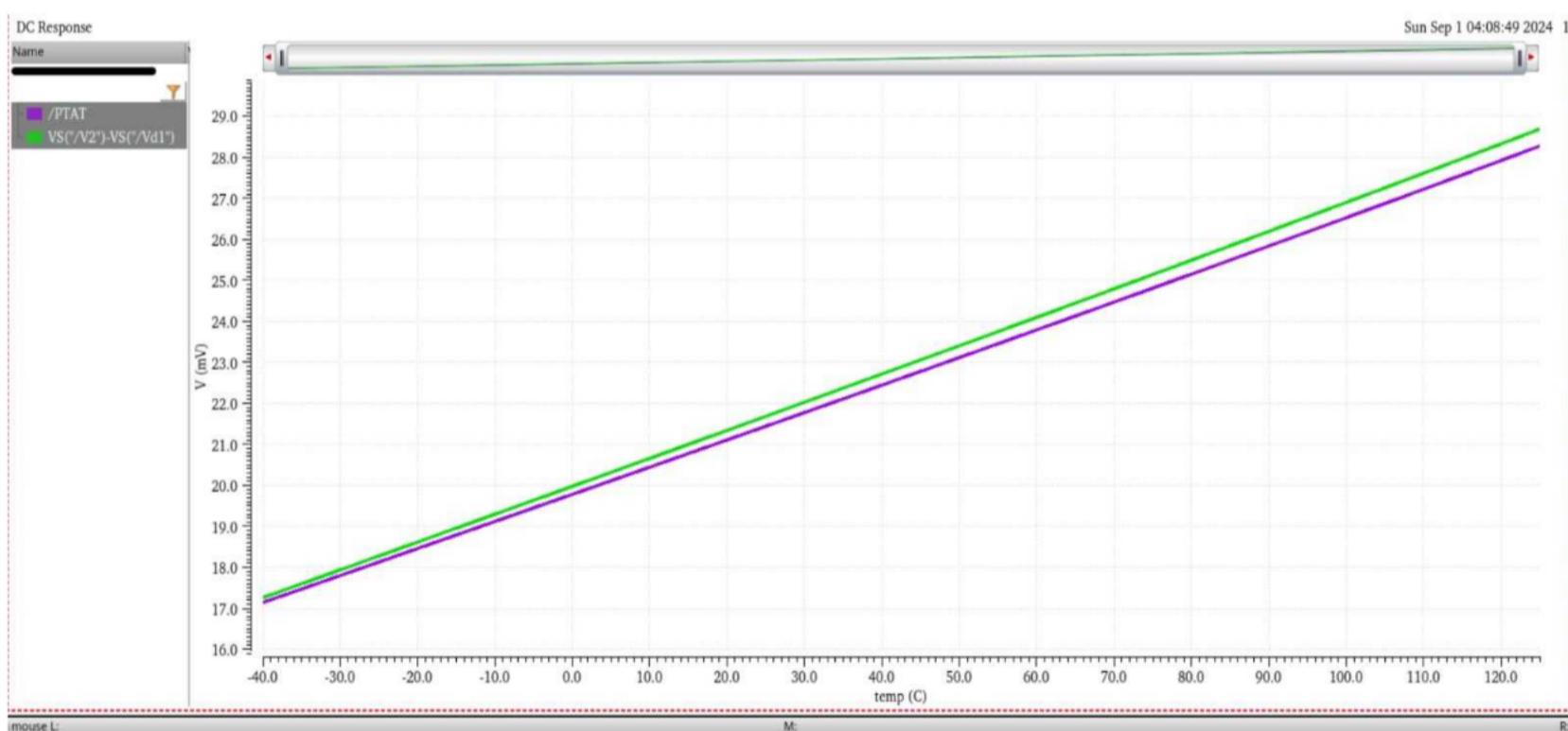
Comparison between $V_2 - V_{d1}$ & PTAT voltage across R_2 :



Adding PTAT & CTAT

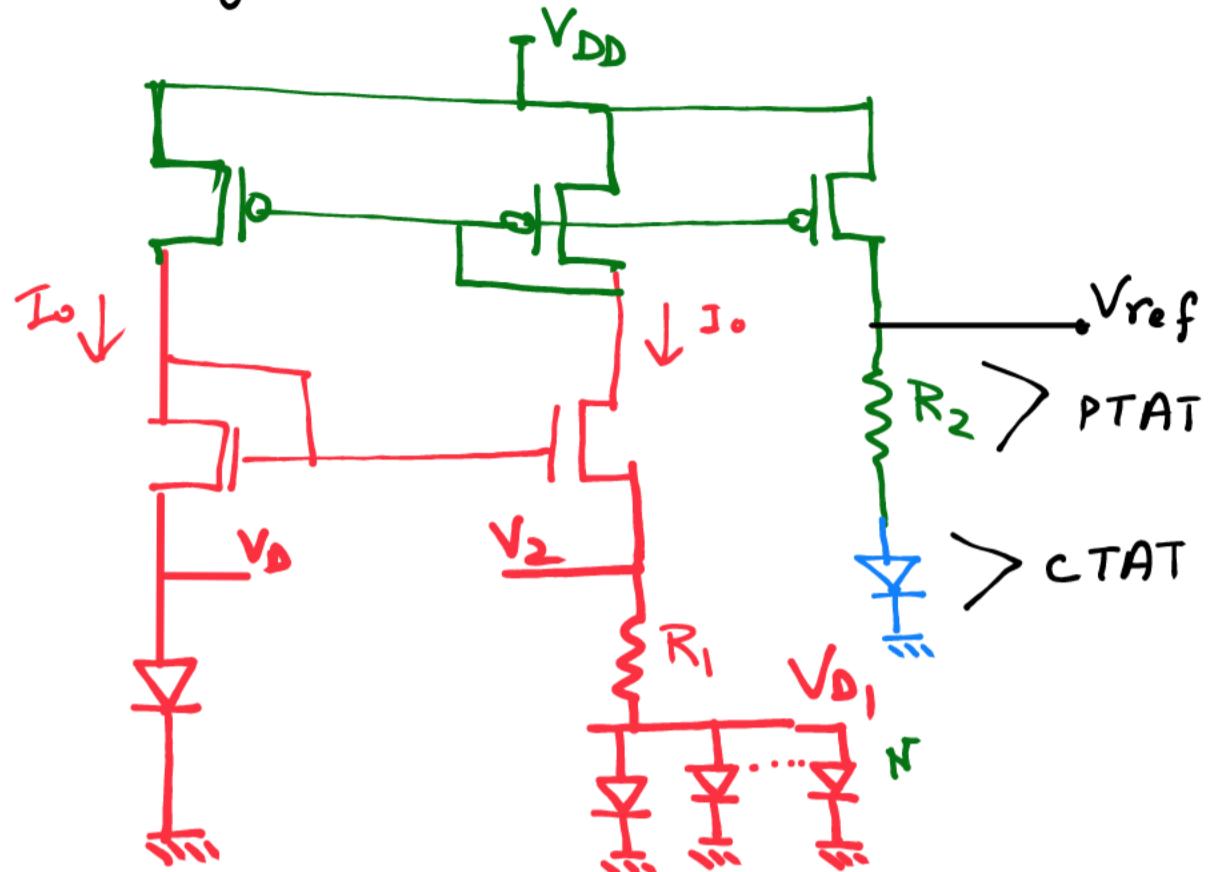


More familiar form (with BJT):

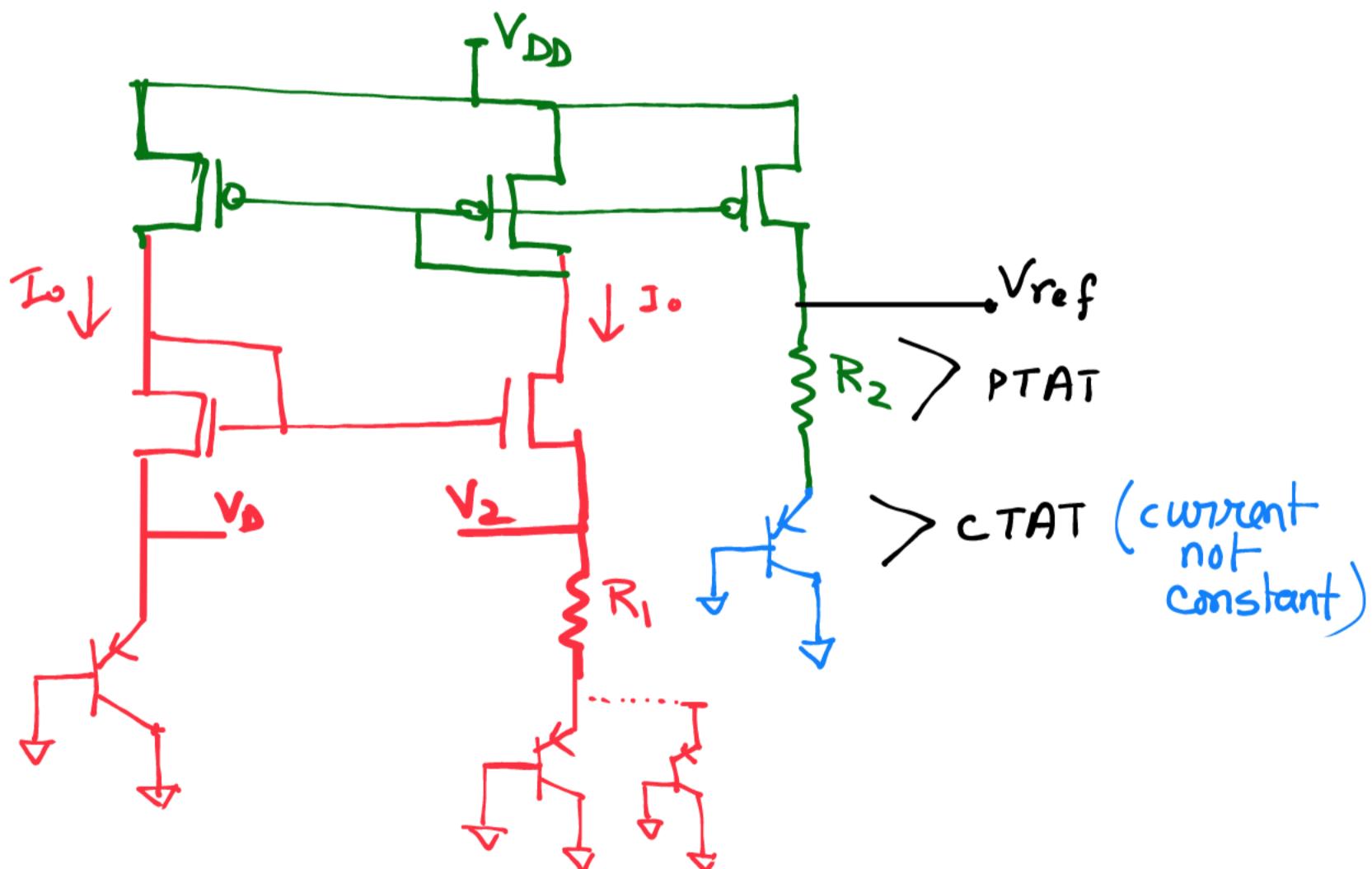

3 issues:

- ① Supply Variation
- ② Current across the BJT is not constant (PTAT in nature)
- ③ α_1 & α_2

Supply Variation:

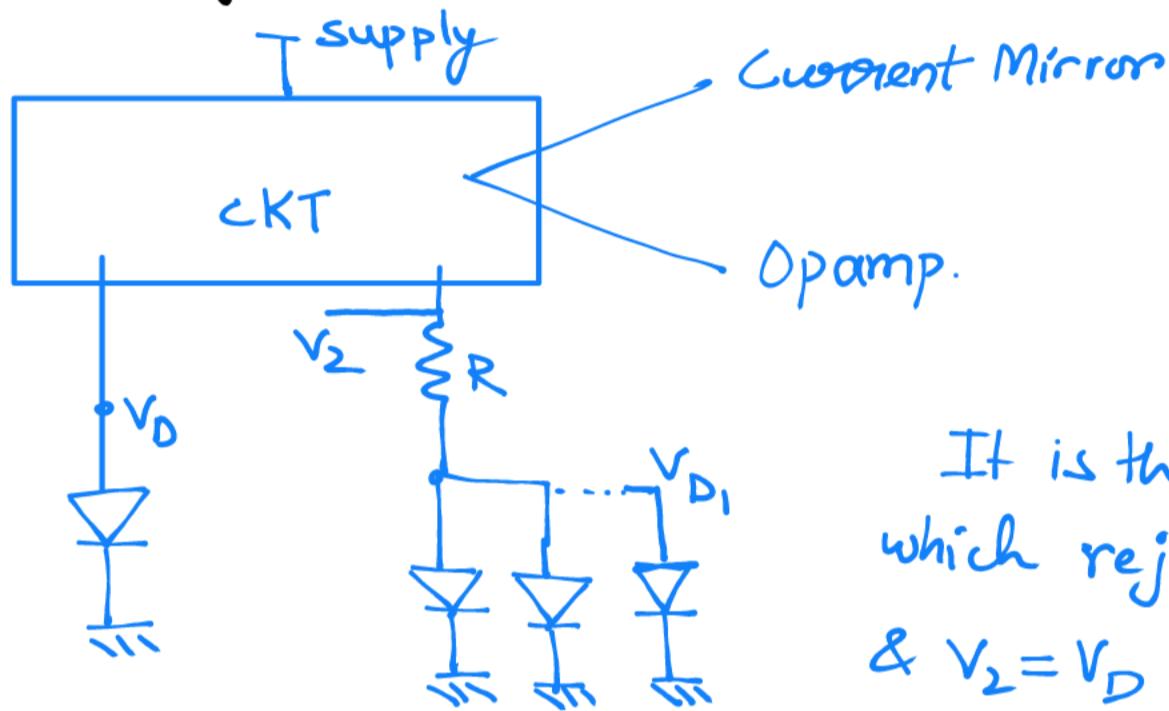

It is the duty of that ckt., which rejects the supply variation
 $\& V_2 = V_D$

$$I_0 = \frac{V_T \ln(n)}{R_1} \rightarrow \text{PTAT current.}$$

$$V_D = V_T \ln\left(\frac{I_0}{I_S}\right)$$

Weak PTAT Strong CTAT

→ effectively CTAT

Now, $I_0 \rightarrow \text{PTAT}$

Considering current as a PTAT:

$$\frac{\partial V_D}{\partial T} = \frac{\partial}{\partial I} \left[V_T \ln \left(\frac{I_0}{I_s} \right) \right]$$

$$= \frac{\partial}{\partial T} V_T \left[\ln(I_0) - \ln(I_s) \right]$$

$$\frac{\partial V_D}{\partial T} = V_T \left[\frac{1}{I_0} \frac{\partial I_0}{\partial T} - \frac{1}{I_s} \frac{\partial I_s}{\partial T} \right] + \left[\ln(I_0) - \ln(I_s) \right] \frac{\partial V_T}{\partial T}$$

only thing
which
remaining

$$I_0 = \frac{\ln(N)}{R_1} \cdot V_T$$

$$\frac{\partial I_0}{\partial T} = \frac{\ln(N)}{R_1} \frac{\partial V_T}{\partial T}$$

$$\frac{\partial I_0}{\partial T} = \frac{k}{q} \frac{\ln(N)}{R_1}$$

$$\frac{\partial I_0}{\partial T} = \frac{\ln(N)}{R_1} \cdot \frac{V_T}{T}$$

$$\boxed{\frac{\partial I_0}{\partial T} = \frac{I_0}{T}} \quad \textcircled{5}$$

Rewriting eq \textcircled{4}: $\frac{\partial I_s}{\partial T} = I_s \left[\frac{4+m}{T} + \frac{E_g}{KT^2} \right] \quad \textcircled{4}$

$$\frac{\partial V_T}{\partial T} = \frac{k}{q} = \frac{V_T}{T} \quad \textcircled{2}$$

$$\begin{aligned} \frac{\partial V_D}{\partial T} &= V_T \left[\frac{1}{I_0} \frac{I_0}{T} - \frac{1}{I_s} I_s \left(\frac{4+m}{T} + \frac{E_g}{KT^2} \right) \right] + \ln \left(\frac{I_0}{I_s} \right) \frac{V_T}{T} \\ &= V_T \left[\frac{1}{T} - \frac{4+m}{T} - \frac{E_g}{KT^2} \right] + \frac{V_T}{T} \ln \left(\frac{I_0}{I_s} \right) \end{aligned}$$

$$\frac{\partial V_D}{\partial T} = V_T \left(\frac{1 - (4+m)}{T} - \frac{E_g}{KT^2} \right) + \frac{V_D}{T}$$

$$\frac{\partial V_D}{\partial T} = \frac{V_D}{T} - \frac{(4+m-1)V_T}{T} - \frac{V_T E_g}{kT^2}$$

$$= \frac{V_D}{T} - \frac{(3+m)V_T}{T} - \frac{E_g/q}{T}$$

$$\frac{\partial V_D}{\partial T} = \frac{V_D - (3+m)V_T - E_g/q}{T} \Rightarrow I_0 \text{ as PTAT}$$

whereas, $\frac{\partial V_D}{\partial T} = \frac{V_D - (4+m)V_T - E_g/q}{T} \Rightarrow I_0 \text{ as const.}$

$\rightarrow -1.88 \text{ mV/}^\circ\text{K}$


$$\begin{aligned}\frac{\partial V_D}{\partial T} &= \frac{0.7 - (3-1.5)25 \text{ m.} - 1.2}{300} \\ &= \frac{0.7 - 39 \text{ mV} - 1.2}{300} \\ &= -1.79 \text{ mV/}^\circ\text{K}\end{aligned}$$

I_0 is PTAT in nature, considering that slope of CTAT is -1.79


whereas I_0 as a constant source, slope found $-1.88 \text{ mV/}^\circ\text{K}$.

Which is more or less same. So this issue is resolved


Design of α_1 & α_2

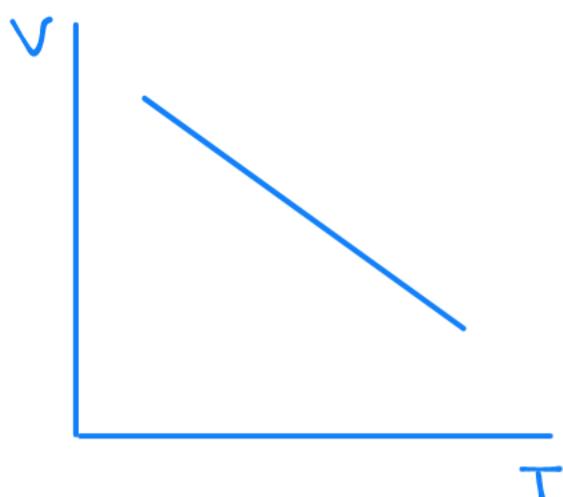

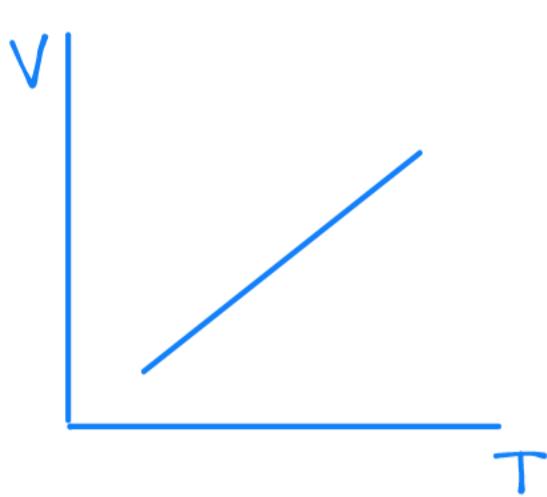Slope -ve
 $-1.6 \text{ mV/}^\circ\text{C}$



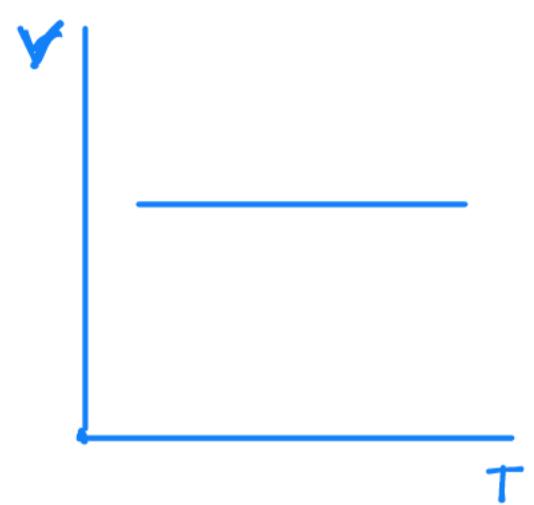Slope +ve
 $85 \mu\text{V/}^\circ\text{C}$



Slope = 0
 $\frac{\partial V_{ref}}{\partial T} = 0$


$$V_{ref} = \alpha_1 \text{ CTAT} + \alpha_2 \text{ PTAT}$$

$$V_{R_2} = \underbrace{\frac{R_2}{R_1} \ln(N)}_{\alpha_1 \text{ Constant}} V_T \xrightarrow{\text{PTAT}}$$

$$V_{ref} = \alpha_1 V_T + \alpha_2 V_D \xrightarrow{\text{B}}$$

$$\frac{\partial V_{ref}}{\partial T} = 0 \Rightarrow \alpha_1 \frac{\partial V_T}{\partial T} + \alpha_2 \frac{\partial V_D}{\partial T} = 0$$
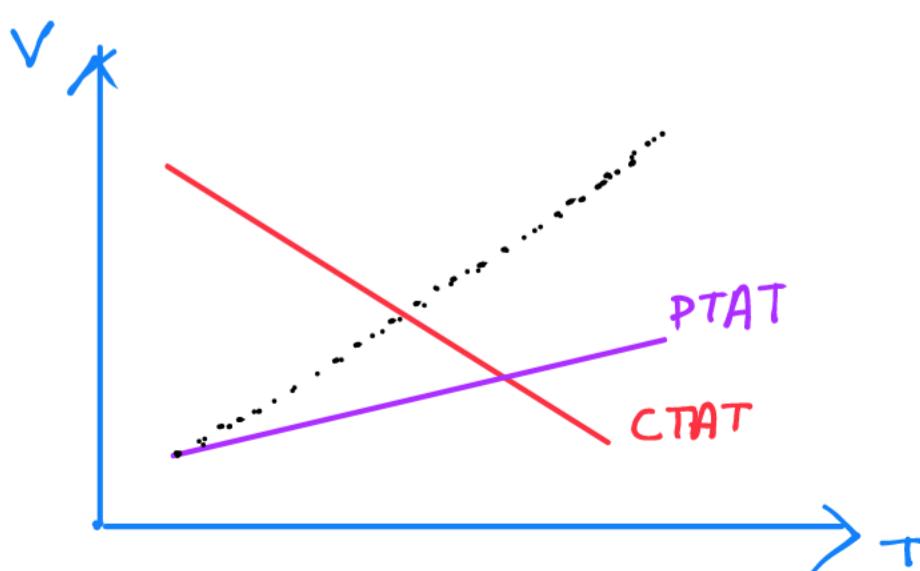
$$\alpha_1 (85 \mu\text{V/}^\circ\text{C}) + \alpha_2 (-1.6 \text{ mV/}^\circ\text{C}) = 0$$



$\alpha_2 = 1$
 $\alpha_1 \rightarrow \text{change}$
 (adjusting PTAT)

$$\alpha_1 \cdot 85\mu V = \alpha_2 \cdot 1.6mV$$

$$\alpha_1 \cdot \underbrace{85\mu V}_{PTAT} = \underbrace{1.6mV}_{CTAT}$$

$$\alpha_1 = \frac{1.6m}{85\mu} = 18.82$$

$$V_{ref} = \alpha_1 \cdot PTAT + CTAT$$

$$V_{ref} = \underbrace{\frac{R_2}{R_1} \ln(N)}_{\alpha_1} \cdot V_T + V_D$$

Derived from
equation A

$$\alpha_1 = 18.82$$

$$V_{ref} = 18.82 V_T + V_D$$

$$\begin{aligned} V_{ref} &= 18.82 \times 26mV + 0.7 \\ &= 1.189 \\ &\approx 1.2 V \end{aligned}$$

$$\text{Now, } \alpha_1 = 18.82 = \frac{R_2}{R_1} \ln(N)$$

(In layout pt. of view $N=8$ is a good value)
"For better matching"

eg: $I_o = 5 \mu A$



$$I_o = \frac{V_T \ln(N)}{R_1}$$

$$\Rightarrow R_1 = \frac{V_T \ln(N)}{I_o} = \frac{26 \text{ mV} \times \ln(2)}{5 \mu A} = 3.6 \text{ k}\Omega$$

Now, $\alpha_1 = 18.82$


$$\alpha_1 = \frac{R_2}{R_1} \ln(N)$$
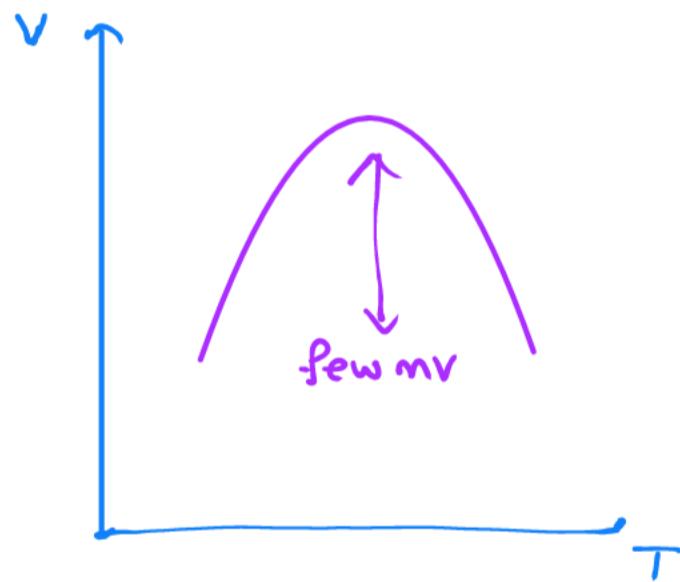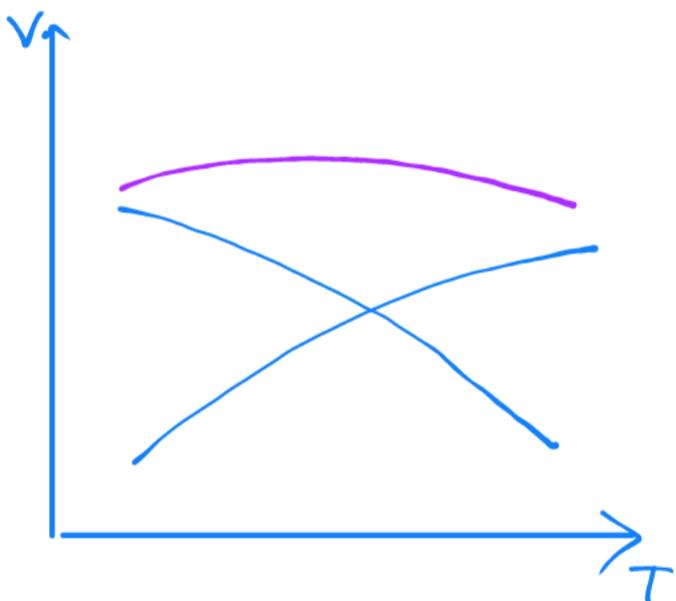
$$\Rightarrow R_2 = \frac{3.6 \times 18.82}{\ln(2)} = 97.7 \text{ k}\Omega$$




This bell shaped curve appears because of the Non-linearity of PTAT & CTAT


Schematic :

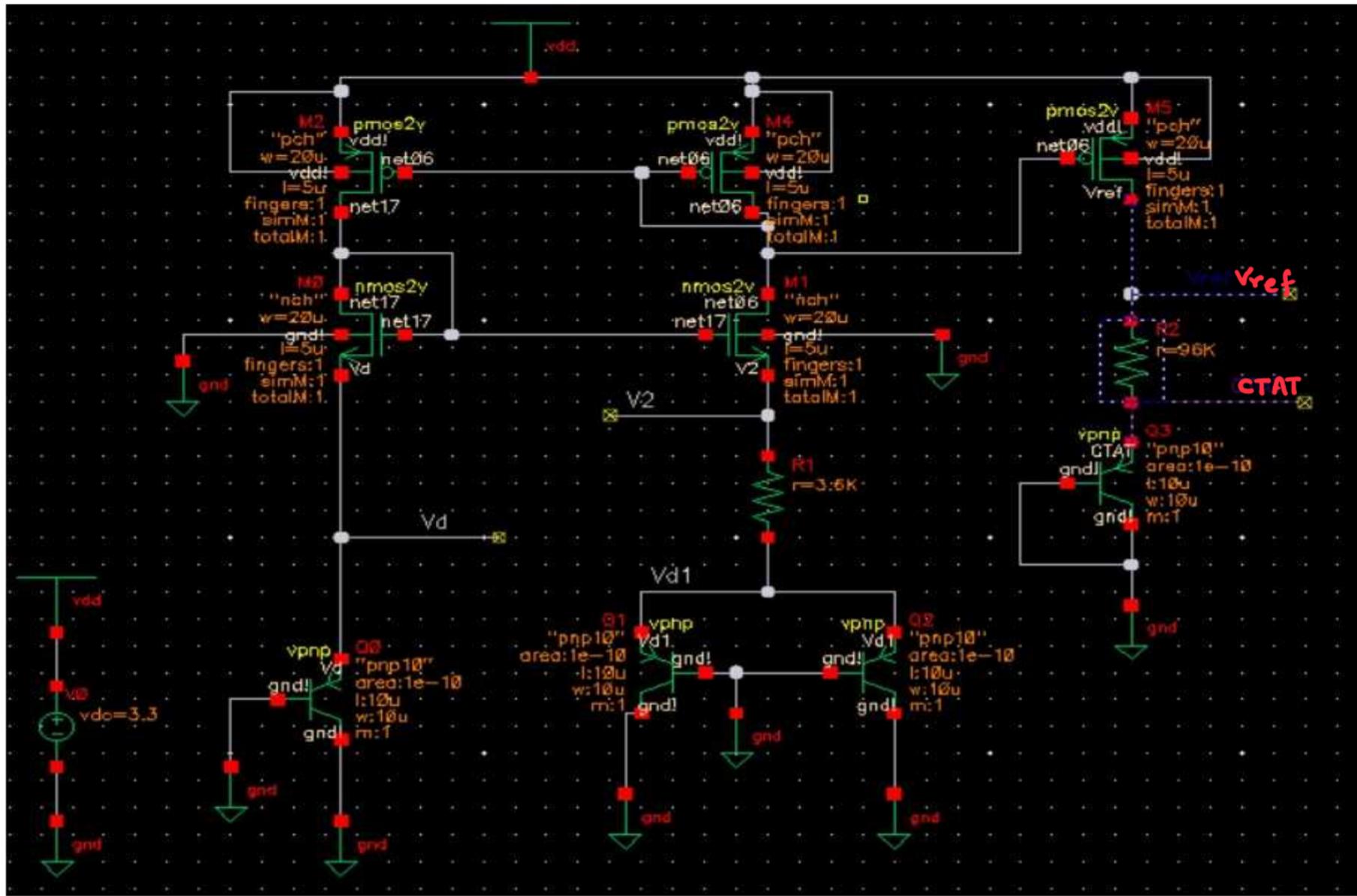

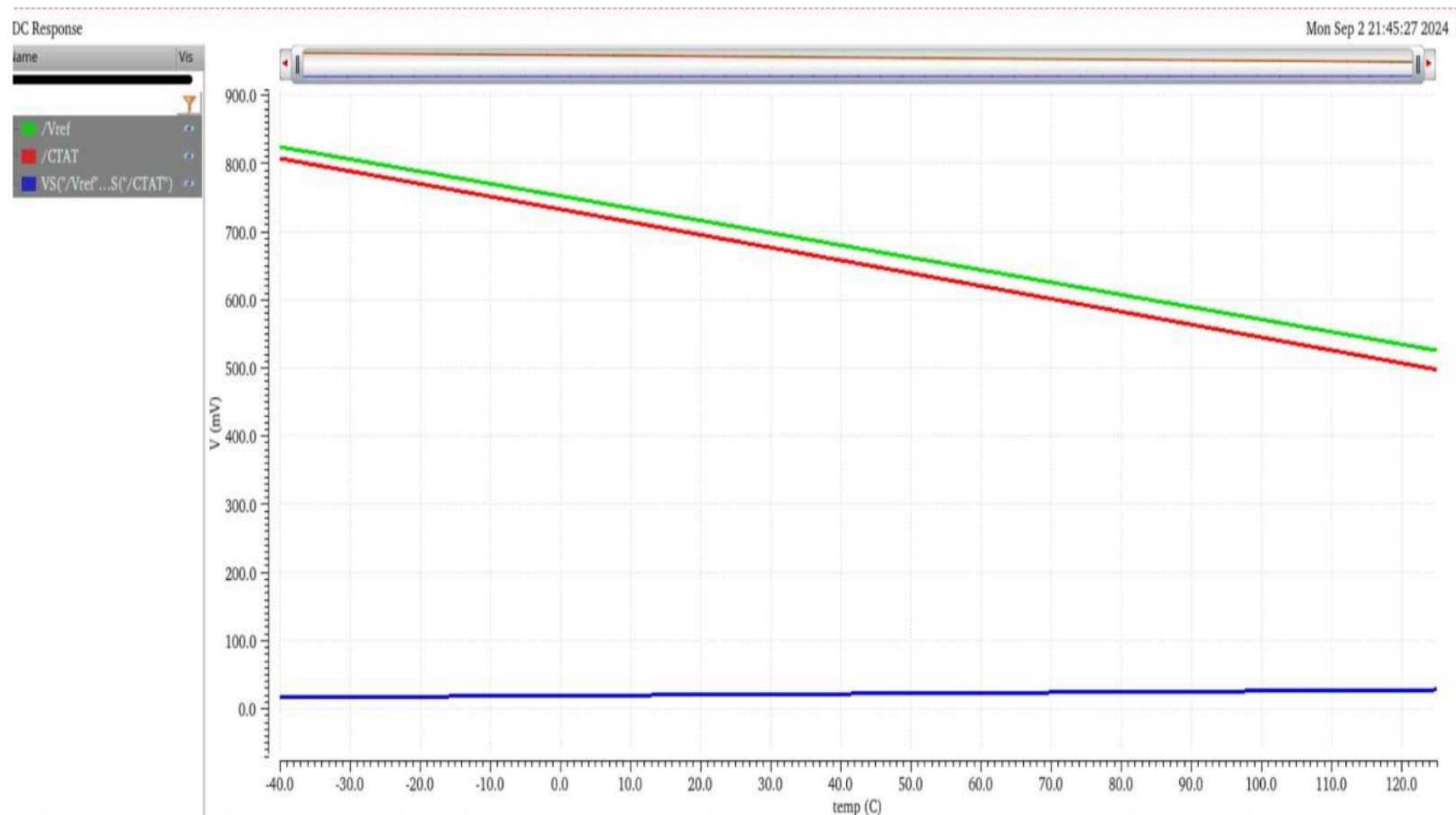
For $R_2 = 3.4\text{ k}\Omega$ CTAT is strong & effectively $V_{ref} \rightarrow CTAT$



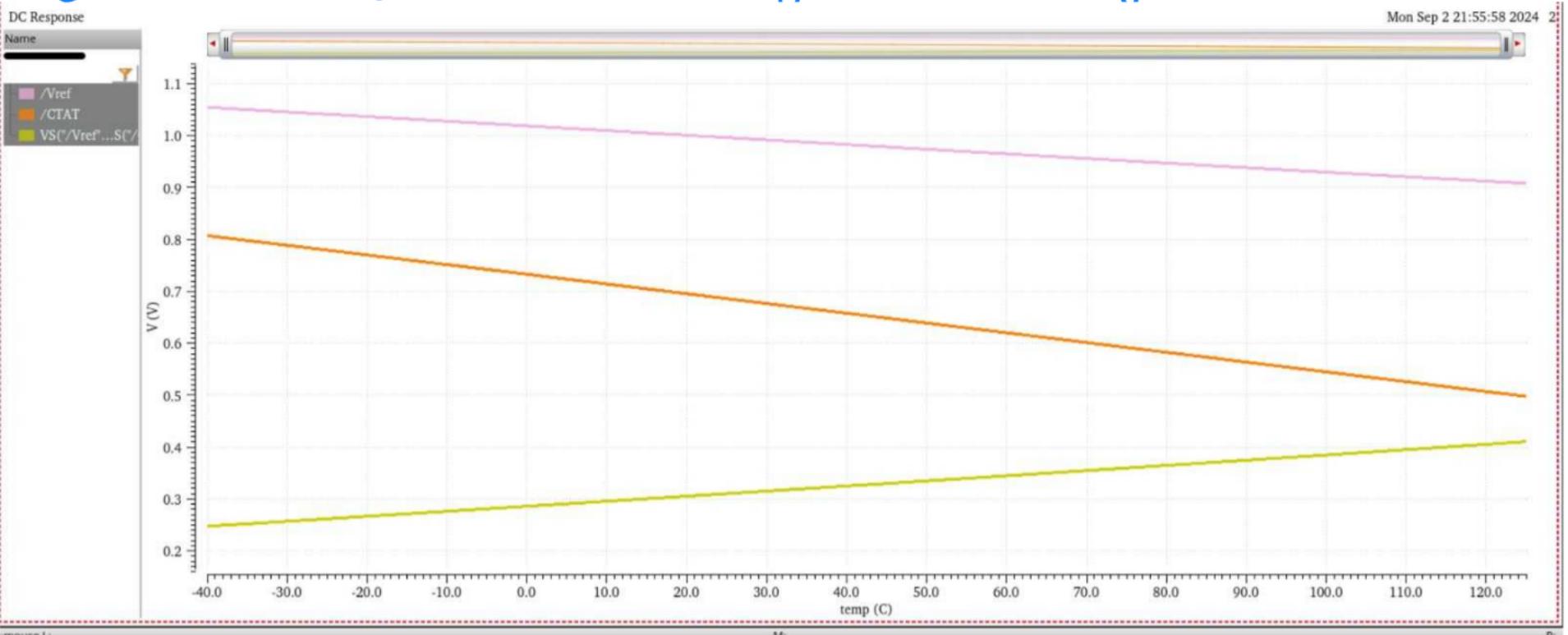
For $R_2 = 50\text{ k}\Omega$ CTAT is strong & effectively $V_{ref} \rightarrow$ CTAT



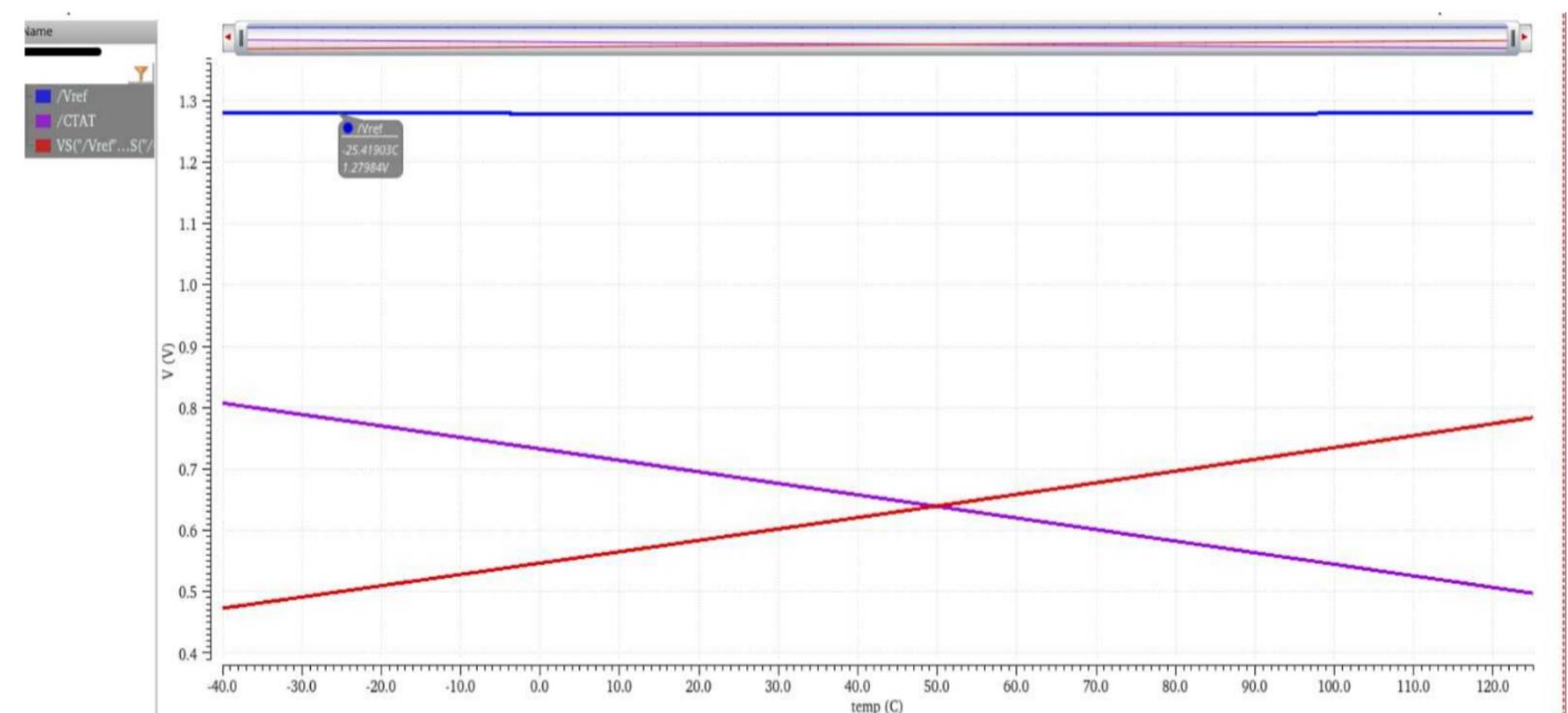For $R_2 = 96\text{ k}\Omega$, $V_{ref} \approx \text{Constant}$.



V_{ref} variation with supply voltage:

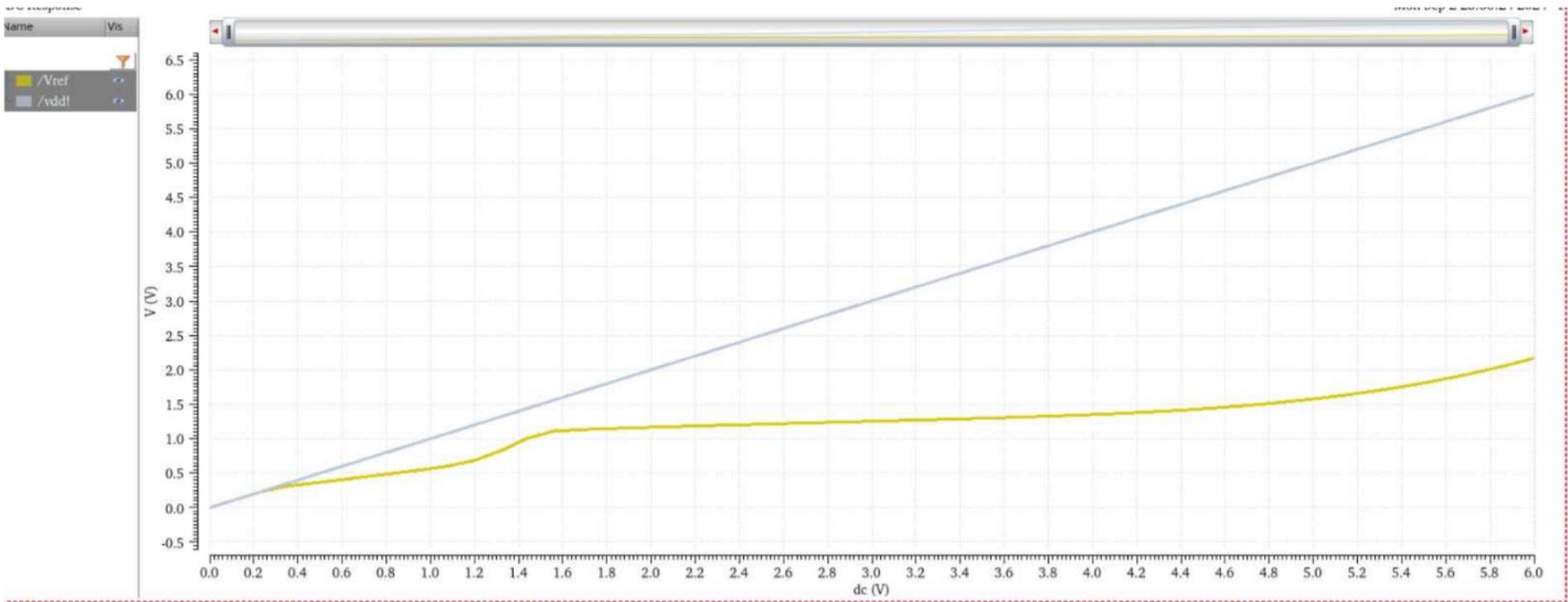

→ for better supply variation rejection → improve the current mirror.

→ cascode structure

(But min supply voltage should
be higher to turn all the
mosfets in saturation)

For higher variation of voltage → need cascode structure

With Cascode Structure:

